

Wentworth Institute of Technology
Comp278 – Computer Architecture

Assignment 1

1. Short Answers (24 pts)

1) Draw the circuit of $(X + Y')Z + X'$

2) Draw the truth table for $(X \text{ NAND } Y)$ and $(X \text{ NOR } Y)$

3) Truth table of XOR and XNOR

2. Number Representation (16 pts) Please show all your work!

1) $156 = (\text{0b} \quad \quad \quad)$

2) $(436) = (\text{0b} \quad \quad \quad)$

3) $(\text{0b110101110}) = (\text{0o} \quad \quad \quad) = \text{decimal} (\quad \quad \quad)$

3. List the truth table of a three-variable exclusive-OR function: $x =$

$A \text{ xor } B \text{ xor } C$. (16 pts) Please show all your work!

A	B	C	B xor C	(A xor (B xor C))
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

4. Boolean Algebra Application (20 pts) Show all your work!

Given the Boolean expression $F = x'y + xyz'$:

a. Derive $F' = y' + xz$

$$F' =$$

b. Show $F'F = 0$

c. Show $F' + F = 1$

5. Logic Diagram and Boolean Expression (24 pts)

Given the Boolean function, $F = xy'z + x'y'z + xyz$

a. Draw the logic diagram using the original Boolean expression.

b. Show with boolean algebra.

$$xy'z + x'y'z + xyz = xz + y'z$$

c. Draw the logic diagram for simplified expression.